

CS 362: Homework 6

Due on April 5, 2024 at 11:59pm

Professor Troy 11:00am


Ryan Magdaleno

rmagd2@uic.edu

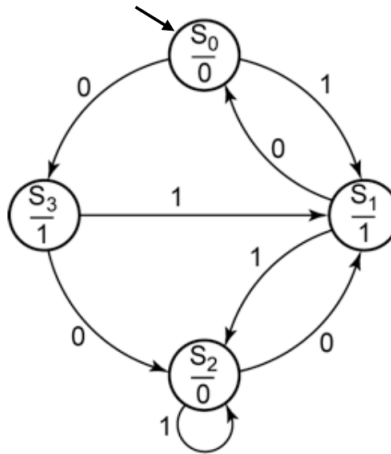Problem 1

Consider the following Finite State Machine. Start State: S0

Output value is under the line below the State number.



Solution

1. Is the above FSM a Moore machine or a Mealy Machine?

Mealy Machine.

2. What is output by the above FSM for the:

Input:

1 0 1 1 0 0 0 1 0 0 1 1

Output:

0 1 0 1 0 1 0 1 1 0 1 1 0

3. Create the truth table to the above FSM. Encode the states using 2 bit binary values:

S0 → 0 0, S1 → 0 1, S2 → 1 0, S3 → 1 1

p1	p0	b	y	n1	n0
0	0	0	0	1	1
0	0	1	0	0	1
0	1	0	1	0	0
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	0	1	0
1	1	0	1	1	0
1	1	1	1	0	1

4. Write out the simplified expressions for the next state and output values. You can use K-maps or boolean algebra to determine simplified expression.

$$n0 = p1p0b + p1p0'b' + p1'p0'b + p1'p0'b'$$

$$n1 = p1'p0'b' + p1p0'b + p1'p0b + p1p0b'$$

Handwritten K-map for $n0$:

	p_1p_0	00	01	11	10
b	0	1	0	0	1
	1	1	0	1	0

Groupings: (00,10), (01,11), (00,10), (01,11), (11,10), (11,01)

$$n0 = p1'p0' + p1p0b + b'p0'$$

Handwritten K-map for $n1$:

	p_1p_0	00	01	11	10
b	0	1	0	1	0
	1	0	1	0	1

Groupings: (00,10), (01,11), (11,10), (11,01), (01,11), (11,01)

$$n1 = p1'p0'b' + p1p0b' + p1'p0b + p1p0'b$$


Handwritten K-map for y :

	p_1p_0	00	01	11	10
b	0	0	1	1	0
	1	0	1	1	0

Groupings: (01,11), (11,10), (11,01), (01,11), (11,01), (11,10)

$$y = p0$$

5. Draw the circuit diagram for the Finite State Machine. Use the format as shown in class and in the zyBooks (and in Q3 below) that contain a state register and a combination logic block.

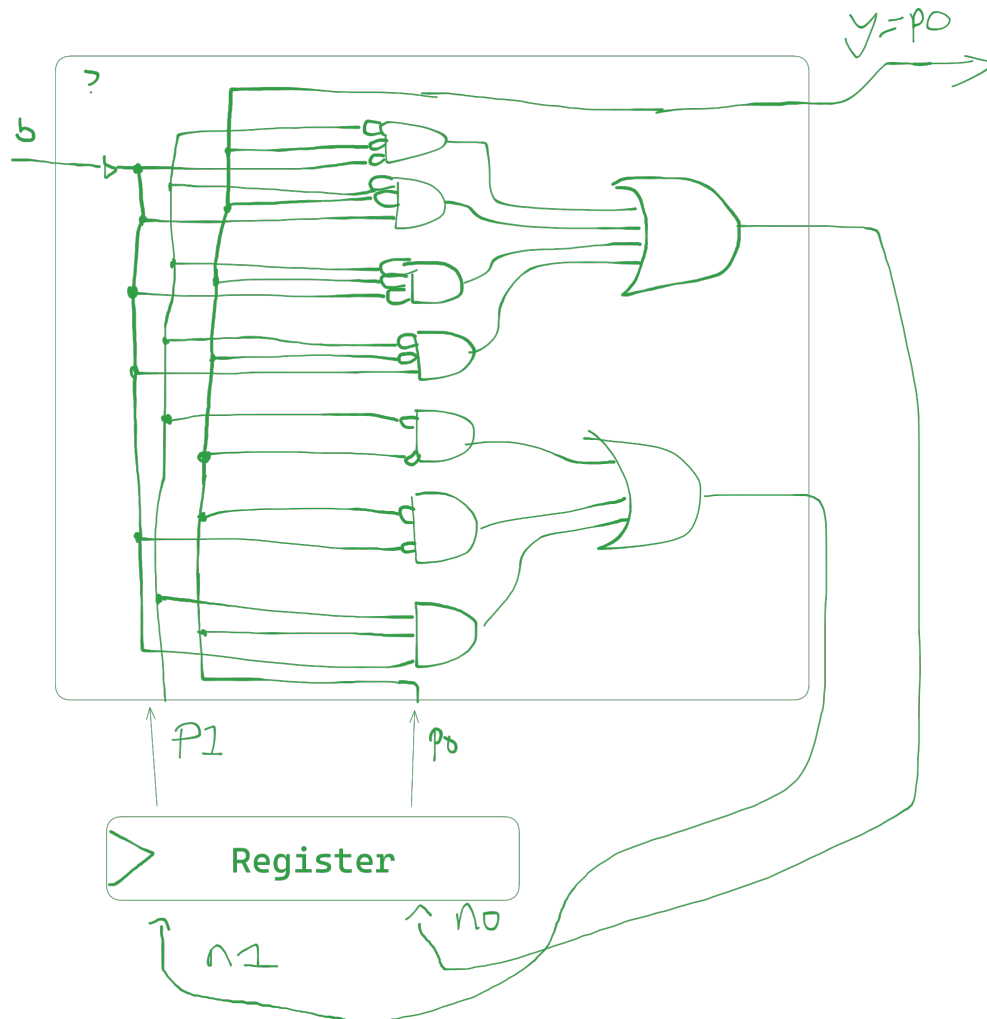


Problem 2

Consider the following Finite State Machine. Start State: S0.

Inputs are listed before the slash on each transition.

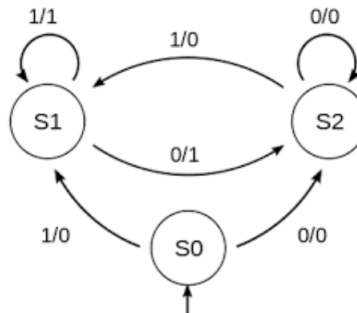Outputs are listed after the slash on each transition.



Solution

1. Is the above FSM a Moore machine or a Mealy machine?

Mealy Machine

2. What is output by the above FSM for:

Input: 1 0 1 1 0 0 0 1 0 0 1 1

Output: 0 1 0 1 1 0 0 0 1 0 0 1

3. Create the truth table to the above FSM. Encode the states using 2 bit binary values:

S0 → 0 0, S1 → 0 1, S2 → 1 0

<i>p1</i>	<i>p0</i>	<i>b</i>	<i>y</i>	<i>n1</i>	<i>n0</i>
0	0	0	0	1	0
0	0	1	0	0	1
0	1	0	1	1	0
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	0	0	1
1	1	0	<i>x</i>	<i>x</i>	<i>x</i>
1	1	1	<i>x</i>	<i>x</i>	<i>x</i>

4. Write out the simplified expressions for the next state and output values. You can use K-maps or boolean algebra to determine simplified expressions.

$\frac{p_1}{b}$	00	01	11	10
0	0	0	X	0
1	1	1	X	1

$$n0 = b$$


$\frac{p_1}{b}$	00	01	11	10
0	1	1	X	1
1	0	0	X	0

$$n1 = b'$$

$\frac{p_1}{b}$	00	01	11	10
0	0	1	X	0
1	0	1	X	0


$$y = b$$

5. Draw the circuit diagram for the Finite State Machine. Use the format as shown in class and in the zyBooks (and in Q3 below) that contain a state register and a combination logic block.

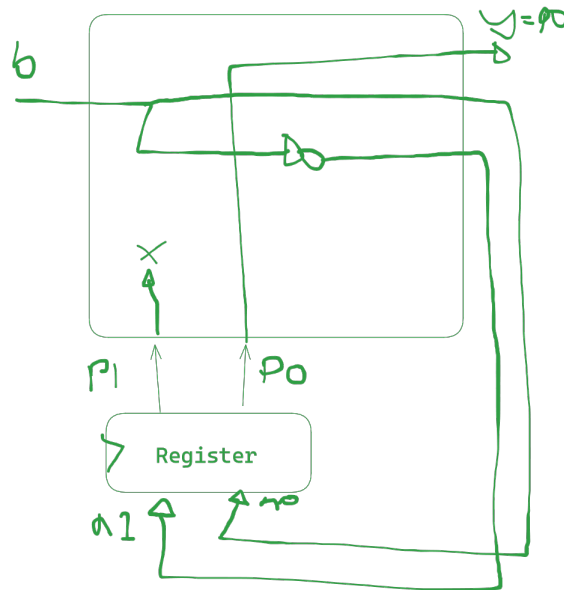




Problem 3

Consider the following circuit:

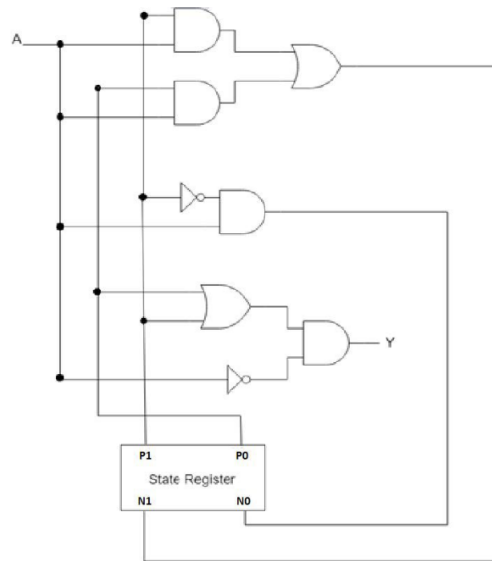

Solution

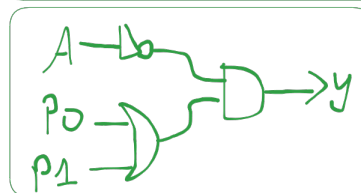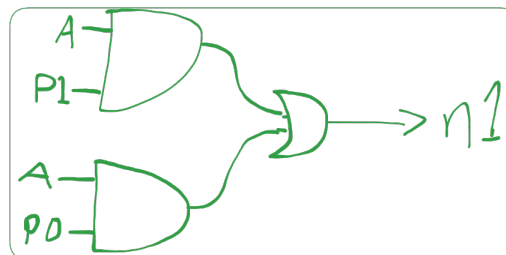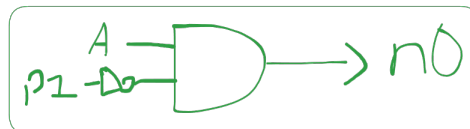- Write the equations for the for the next state and output values from the above controller.



$$n0 = p1' a$$

$$n1 = p1 a + p0 a$$

$$y = A' \cdot (p0 + p1)$$


2. Create the truth table for the above circuit:

$p1$	$p0$	A	Y	$n1$	$n0$
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	1	0	0
0	1	1	0	1	1
1	0	0	1	0	0
1	0	1	0	1	0
1	1	0	1	0	0
1	1	1	0	1	0

3. What information needed for drawing a Finite State Machine is not included in the Truth Table and will need to be assumed?

We need to assume some start state, I will divide the truth table into four states, S_0 will be the first two rows in the table, this will be our start state.

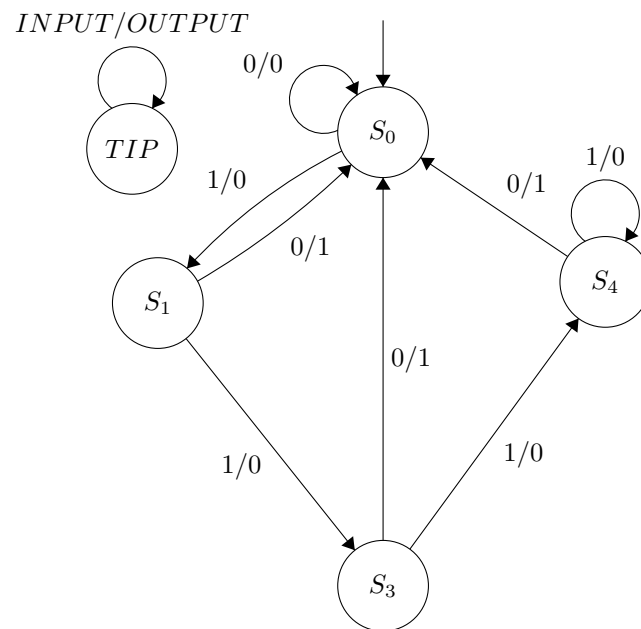4. Draw the Finite State Machine that is represented by the circuit:



5. Is the Finite State Machine a Moore machine or a Mealy machine?

Mealy machine.

6. What is output by the above FSM for:

Input: 1 0 1 1 0 0 0 1 0 0 1 1

Output: 0 1 0 0 1 0 0 0 1 0 0 0