

CS 362 :: Homework 2


Ryan Magdaleno

February 16, 2024

Problem 1. Write the truth table for the CMOS Circuit given below and specify which logic gate it represents.

Solution ::


a) ::

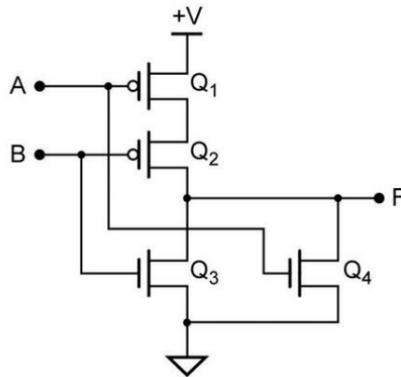

A	B	Q_1	Q_2	Q_3	Q_4	F
0	0	1	1	0	0	1
0	1	1	0	1	0	0
1	0	0	1	0	1	0
1	1	0	0	1	1	0

This circuit represents a NOR gate.

b) ::

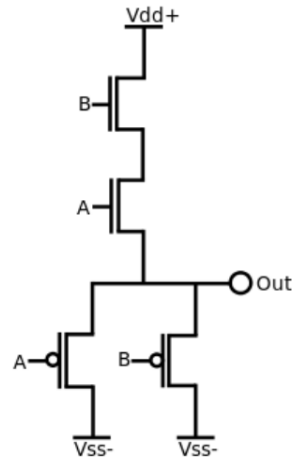


A	B	Out
0	0	0
0	1	0
1	0	0
1	1	1

This circuit represents an AND gate.

Write the truth table for the CMOS Circuit given below and specify the equation it represents.

a) ::

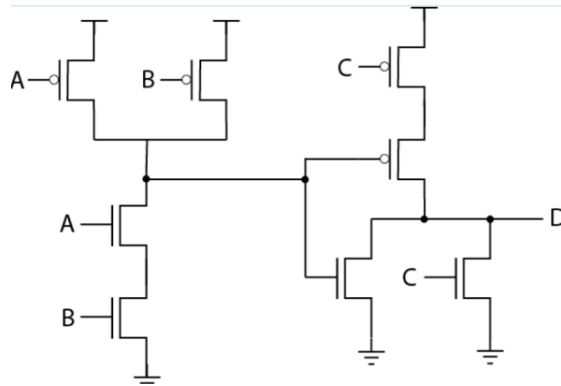


A	B	C	D
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

This circuit table can be represented like so:

$$D = ABC'$$

b) ::

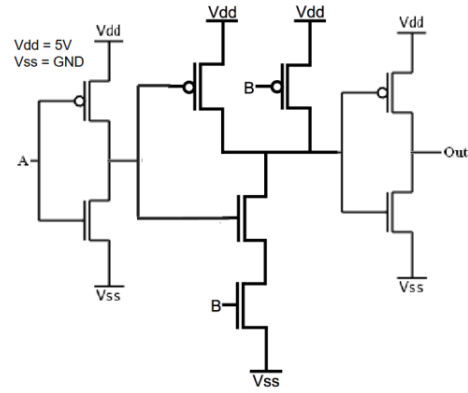

A	B	Out
0	0	0
0	1	1
1	0	0
1	1	0


This circuit table can be represented like so:

$$Out = A'B$$


Problem 2. NAND gates and NOR gates are two types of Universal Gates. Represent each equation as a circuit using only **a single type** of a Universal Gate. I.E. Each answer must contain only NAND gates or must contain only NOR gates. Assume literals are not available in complemented form.

Solution ::

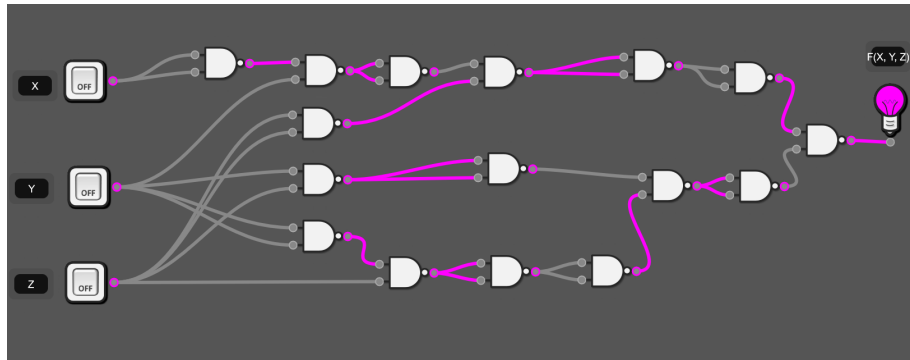
a) $F(x, y, z) = \bar{y}\bar{z} + \bar{y}z + \bar{x}y\bar{z}$



b) $F(x, y, z) = (x' + y) \cdot (y + z) \cdot (x' + y' + z)$

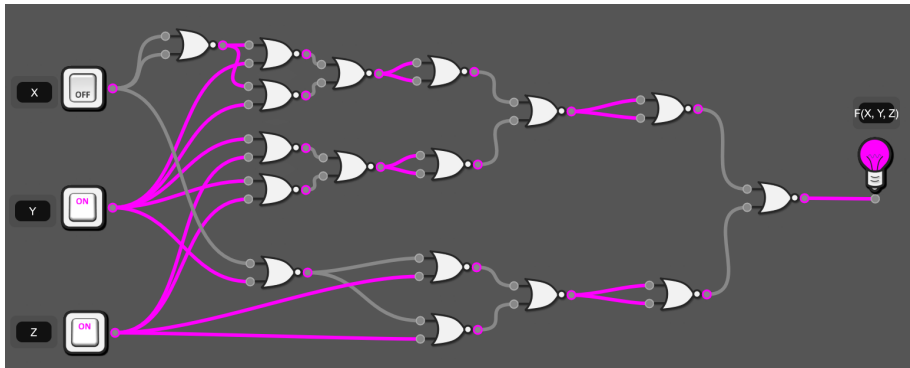

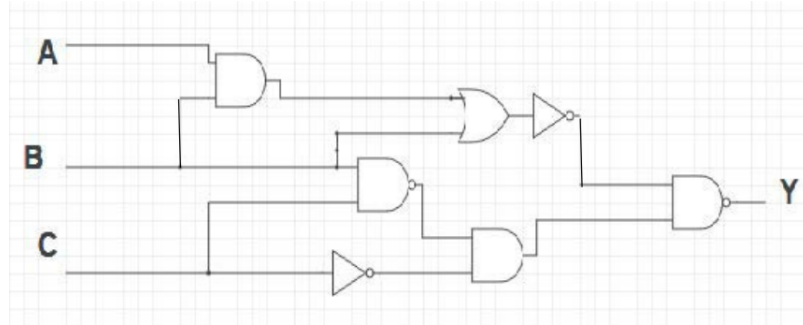Problem 3. Write the truth table and equation for the following circuit diagram. Do not do any simplification on the equation when written for your answer.



Solution ::

A	B	C	Y
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Equation:

$$Y = ABC + ABC' + AB'C + A'BC + A'BC' + A'B'C$$

The following Boolean Properties are to be used and referenced by name for each/every step to receive full credit when you “show your work” during the remaining problems in this homework.

$$a \cdot (b + c) = a \cdot a + a \cdot c = \text{Distributive (AND)}$$

$$a + (b \cdot c) = (a + b) \cdot (a + c) = \text{Distributive (OR)}$$

$$a \cdot b = b \cdot a = \text{Commutative}$$

$$a + b = b + a$$

$$(a \cdot b) \cdot c = a \cdot (b \cdot c) = \text{Associative}$$

$$(a + b) + c = a + (b + c)$$

$$a \cdot a' = 0 = \text{Complement (AND)}$$

$$a + a' = 1 = \text{Complement (OR)}$$

$$a \cdot 1 = a = \text{Identity (AND)}$$

$$a + 0 = a = \text{Identity (OR)}$$

$$a \cdot 0 = 0 = \text{Null elements}$$

$$a + 1 = 1$$

$$a \cdot a = a = \text{Idempotent}$$

$$a + a = a$$

$$(a')' = a = \text{Involution}$$

$$(a \cdot b)' = (a' + b') = \text{DeMorgan's (AND)}$$

$$(a + b)' = (a' \cdot b') = \text{DeMorgan's (OR)}$$

Problem 4. Expand the following equations to sum-of-minterm equations

Solution ::

a) $ab' + a'bc$ (assume literals are a, b, c)

$$\begin{aligned} ab'(1) + a'bc & \quad (\text{Null elements}) \\ ab'(c' + c) + a'bc & \quad (\text{Complement (OR)}) \\ ab'c + ab'c + a'bc & \quad (\text{Distributive (AND)}) \end{aligned}$$

b) $ac + bc + a'b$ (assume literals are a, b, c)

$$\begin{aligned} ac(1) + bc(1) + a'b(1) & \quad (\text{Null elements}) \\ ac(b + b') + bc(a + a') + a'b(c' + c) & \quad (\text{Complement (OR)}) \\ ab'c + abc + abc + a'bc + a'bc' + a'bc & \quad (\text{Distributive (AND)}) \end{aligned}$$

c) $ad' + b'c$ (determine literals based on original equation)

$$\begin{aligned} ad'(1)(1) + b'c(1)(1) & \quad (\text{Null elements}) \\ ad'(b + b')(c + c') + b'c(a + a')(d + d') & \quad (\text{Complement (OR)}) \\ ad'(bc + bc' + b'c' + b'c) + b'c(a'd' + a'd + ad' + ad) & \quad (\text{Distributive (AND)}) \\ abcd' + abc'd' + abc'd' + ab'c'd' + ab'cd + ab'cd' + a'b'cd + a'b'cd' & \quad (\text{Distributive (AND)}) \end{aligned}$$

Problem 5. Determine if the two equations (y & z) are equivalent by expanding each to a sum-of-minterm equation. Show your work.

Solution ::

a) $y = ab' + a'b + c$
 $z = ab'c' + ac + a'bc + a'c$

$$y = ab'c + ab'c' + a'bc + a'bc' + a'b'c + a'bc' + ab'c + abc$$

$$z = a'b'c + a'bc + abc + ab'c + a'bc' + ab'c'$$

y and z are equivalent equations.

b) $y = a'b' + bc'$
 $z = a'c' + b'c$

$$y = a'bc'd' + a'bc'd + abc'd' + abc'd + a'b'c'd' + a'b'c'd + a'b'cd' + a'b'cd$$

$$z = a'b'cd' + a'b'cd + ab'cd' + ab'cd + a'b'c'd' + a'b'c'd + a'bc'd' + a'bc'd$$

$$y = abc'd + abc'd'$$

$$z = ab'cd + ab'cd'$$

y and z are not equivalent equations.

Problem 6a. Convert the truth table to sum-of-minterms expression.
Show your work.

a	b	c	F	minterm
0	0	0	1	
0	0	1	1	
0	1	0	0	
0	1	1	0	
1	0	0	1	
1	0	1	0	
1	1	0	1	
1	1	1	1	

Solution ::

$$\begin{aligned}
 &= a'b'c' + a'b'c + ab'c' + abc' + abc \\
 &= (m_0 + m_1 + m_4 + m_6 + m_7) \\
 F(a, b, c) &= \sum (0, 1, 4, 6, 7)
 \end{aligned}$$

Problem 6b. Convert the truth table to product-of-maxterms expression.
Show your work.

a	b	c	F	maxterm
0	0	0	0	
0	0	1	1	
0	1	0	0	
0	1	1	1	
1	0	0	1	
1	0	1	1	
1	1	0	0	
1	1	1	1	

Solution ::

$$\begin{aligned}
 &= (a' + b' + c) \cdot (a + b' + c) \cdot (a + b + c) \\
 &= (M_0 \cdot M_2 \cdot M_6) \\
 F(a, b, c) &= \Pi M(0, 2, 6)
 \end{aligned}$$

Problem 6c. Express the truth table to **either a sum-of-minterms expression or a product-of-maxterms expression**.

Choose the one with the simplest expression (i.e. fewest number of total literals). Show your work

a	b	c	F	minterm
0	0	0	1	
0	0	1	1	
0	1	0	0	
0	1	1	0	
1	0	0	1	
1	0	1	0	
1	1	0	1	
1	1	1	1	

Solution ::

$$\begin{aligned}
 &= (a' + b + c' + (a + b + c)) \\
 &= (M_0 \cdot M_5), \\
 F(a, b, c) &= \Pi M(0, 5)
 \end{aligned}$$

Problem 6d. Express the truth table to either a sum-of-minterms expression or a product-of-maxterms expression. Choose the one with the simplest expression (i.e. fewest number of total literals). Show your work.

a	b	c	F	minterm	maxterm
0	0	0	0		
0	0	1	0		
0	1	0	1		
0	1	1	0		
1	0	0	0		
1	0	1	0		
1	1	0	1		
1	1	1	0		

Solution ::

$$\begin{aligned}
 &= abc' + ab'c \\
 &= (m_2, m_6) \\
 F(a, b, c) &= \sum m(2, 6)
 \end{aligned}$$

Problem 7. Simplify the sum-of-minterms expression below to sum-of-products form using Boolean Algebra properties. The “simplest” expression has the fewest literals. Show your work. (I’m super lost on this one)

Solution ::

$$\begin{aligned}
 \text{a) } F(x, y, z) &= x'y'z' + x'yz + xy'z' + xyz' + xyz \\
 &= x'yz + y'z'(x' + x) + xy(x' + z) \quad \text{Null elements and comp. (OR)} \\
 &= xy + y'z' + x'yz \\
 &= y(x'y + x) + y'z' \quad \text{Dist. (AND)}
 \end{aligned}$$

$$\begin{aligned}
 \text{b) } F(x, y, z) &= xyz' + x'y'z + x'y'z' + x'yz + x'yz' \\
 &= xyz' + x'y'(x + z') + z'y(x + x') \\
 &= xyz' + x'y'(1) + x'y(1) \quad \text{Null elements} \\
 &= xyz' + x'y' + x'y \quad \text{complement (OR)} \\
 &= x'y' + y(x' + z'x) \quad \text{Distributive (AND)} \\
 &= x'y' + y((x + 1) \cdot z') \quad \text{Null elements} \\
 &= y'x + z'y
 \end{aligned}$$

: (Ran out of time,