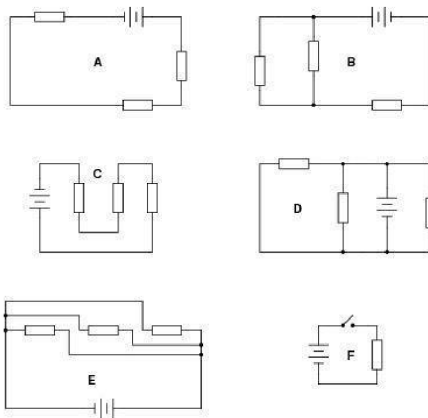


CS362 :: Homework 1

Ryan Magdaleno

February 2, 2024

Problem 1. Consider the following circuits. The resistors are shown as empty rectangles in the diagrams below.



Solution ::

a) Identify which of these circuits contains resistors only in series.

A, C, F

b) Identify which of these circuits contains resistors only in parallel.

D, E


c) Identify which of these circuit contain resistors in a combination of both series and parallel.

B

Problem 2. Calculate appropriate values for each of the following series circuits. Show your work.

Solution ::

a) ::

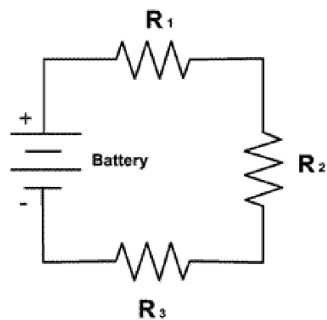

Assume that for the circuit:

The battery is 12V

R_1 is $1\text{k}\Omega$

R_2 is $2\text{k}\Omega$

R_3 is $4\text{k}\Omega$

Determine the total Resistance for the circuit.

$$R_T = R_1 + R_2 + R_3$$

$$R_T = 1\text{k}\Omega + 2\text{k}\Omega + 4\text{k}\Omega$$

$$R_T = 7\text{k}\Omega$$

Determine the Current for the entire circuit.

$$I = \frac{V}{R_T}$$

$$I = \frac{12}{7000}$$

Determine the Voltage Drop across each of the 3 resistors.


$$V_1 = IR_1 = \frac{12}{7000} \cdot 1000 \approx 1.71429V$$

$$V_2 = IR_2 = \frac{12}{7000} \cdot 2000 \approx 3.42857V$$

$$V_3 = IR_3 = \frac{12}{7000} \cdot 4000 \approx 6.85714V$$

$$12V = V_1 + V_2 + V_3$$

b) ::

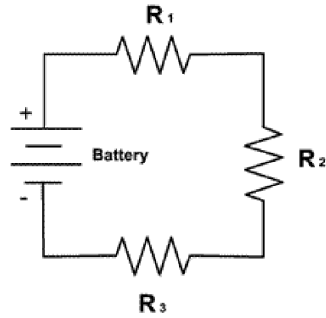

Assume that for the circuit:

The battery is 5V

R1 is 10Ω

R2 is 20Ω

R3 is 30Ω

Determine the total Resistance for the circuit.

$$R_T = R_1 + R_2 + R_3$$

$$R_T = 10\ \Omega + 20\ \Omega + 30\ \Omega$$

$$R_T = 60\ \Omega$$

Determine the Current for the entire circuit.

$$I = \frac{V}{R_T}$$

$$I = \frac{5}{60}$$

$$I = 0.08\bar{3}A$$

Determine the Voltage Drop across each of the 3 resistors.

$$V_1 = IR_1 = 0.08\bar{3} \cdot 10 = 0.8\bar{3}V$$

$$V_2 = IR_2 = 0.08\bar{3} \cdot 20 = 1.6\bar{6}V$$


$$V_3 = IR_3 = 0.08\bar{3} \cdot 30 = 2.5V$$

$$5V = V_1 + V_2 + V_3$$

Problem 3. Calculate appropriate values for each of the following parallel circuits. Show your work.

Solution ::

a) ::

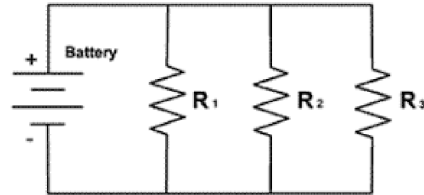

Assume that for the circuit:

The battery is 12V

R_1 is 10Ω

R_2 is 20Ω

R_3 is 40Ω

Determine the total Resistance for the circuit.

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$\frac{1}{R_T} = \frac{1}{10} + \frac{1}{20} + \frac{1}{40}$$

$$\frac{1}{R_T} = 0.175 \Omega$$

$$R_T = \frac{40}{7} \approx 5.71429 \Omega$$

Determine the Current for the entire circuit.

$$I_{in} = \frac{V}{R_T}$$

$$I_{in} = \frac{12}{\frac{40}{7}}$$

$$I_{in} = 2.1 A$$

Determine the Current passing through each of the 3 resistors.


$$I_i = \left(\frac{R_T}{R_i} \right) \cdot I_{in}$$

$$I_1 = \left(\frac{\approx 5.71429}{10} \right) \cdot 2.1 = 1.2 A$$

$$I_2 = \left(\frac{\approx 5.71429}{20} \right) \cdot 2.1 = 0.6 A$$

$$I_3 = \left(\frac{\approx 5.71429}{40} \right) \cdot 2.1 = 0.3 A$$

b) ::

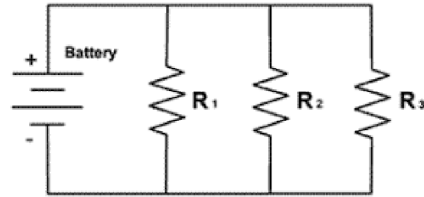

Assume that for the circuit:

The battery is 5V
R1 is 5Ω
R2 is 2Ω
R3 is 3Ω

Determine the total Resistance for the circuit.

$$\begin{aligned}\frac{1}{R_T} &= \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \\ \frac{1}{R_T} &= \frac{1}{5} + \frac{1}{2} + \frac{1}{3} \\ \frac{1}{R_T} &= 1.0\bar{3} \Omega \\ R_T &= \frac{30}{31} \approx 0.96774 \Omega\end{aligned}$$

Determine the Current for the entire circuit.

$$\begin{aligned}I_{in} &= \frac{V}{R_T} \\ I_{in} &= \frac{5}{\frac{30}{31}} = \frac{31}{6} \\ I_{in} &= 5.1\bar{6} A\end{aligned}$$

Determine the Current passing through each of the 3 resistors.


$$\begin{aligned}I_i &= \left(\frac{R_T}{R_i} \right) \cdot I_{in} \\ I_1 &= \left(\frac{\approx 0.96774}{5} \right) \cdot 5.1\bar{6} = 1 A \\ I_2 &= \left(\frac{\approx 0.96774}{2} \right) \cdot 5.1\bar{6} = 2.5 A \\ I_3 &= \left(\frac{\approx 0.96774}{3} \right) \cdot 5.1\bar{6} = 1.6 A\end{aligned}$$

Problem 4. Calculate appropriate values for each of the following circuits.

Show your work.

Solution ::

a) ::

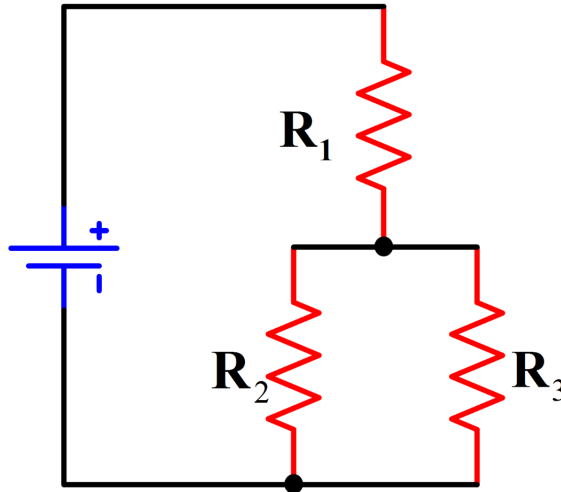

Assume for the circuit:

The battery is 12v

R1 is $2\text{k}\Omega$

R2 is $4\text{k}\Omega$

R3 is $8\text{k}\Omega$

Determine the total Resistance for the circuit.

$$R_T = 2000 + \frac{1}{\frac{1}{4000} + \frac{1}{8000}}$$

$$R_T = \frac{14000}{3} = 4666.\bar{6} \Omega$$

Determine the Current for the entire circuit.

$$I_{in} = \frac{12}{4666.\bar{6}}$$

$$I_{in} = \frac{9}{3500} \approx 0.00257 A$$


Determine the Current passing through each of the 3 resistors.

$$I_1 = I_{in} \approx 0.00257 A$$

$$I_2 = 0.00257 \cdot \left(\frac{2666.6}{4000} \right) \approx 0.00171 A$$

$$I_3 = 0.00257 \cdot \left(\frac{2666.6}{8000} \right) \approx 0.00086 A$$

b) ::

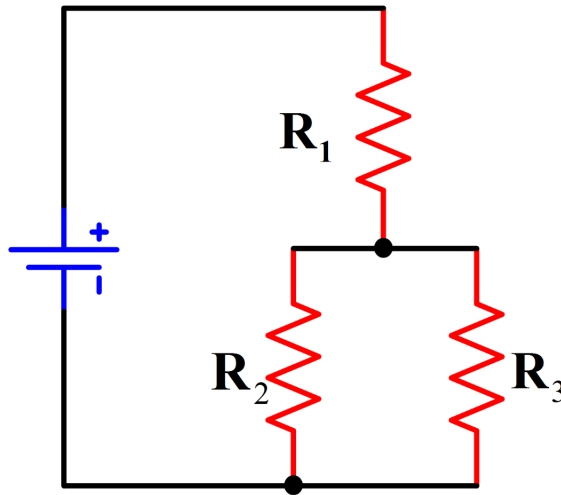

Assume for the circuit:

The battery is 5v

R1 is 10Ω

R2 is 20Ω

R3 is 40Ω

Determine the total Resistance for the circuit.

$$R_T = 10 + \frac{1}{\frac{1}{20} + \frac{1}{40}}$$

$$R_T = \frac{70}{3} = 23.\bar{3}\Omega$$

Determine the Current for the entire circuit.

$$I_{in} = \frac{5}{23.\bar{3}}$$

$$I_{in} = \frac{3}{14} \approx 0.21429A$$


Determine the Current passing through each of the 3 resistors.

$$I_1 = I_{in} \approx 0.21429A$$

$$I_2 = \frac{3}{14} \cdot \left(\frac{13.\bar{3}}{20}\right) \approx 0.00143A$$

$$I_3 = \frac{3}{14} \cdot \left(\frac{13.\bar{3}}{40}\right) \approx 0.00071A$$

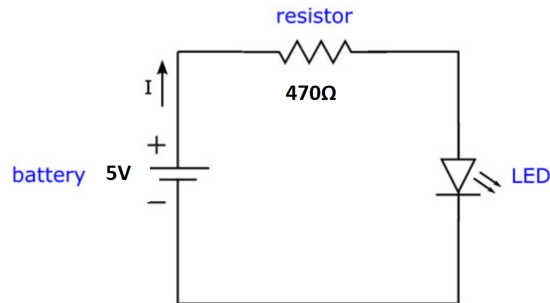Problem 5a. You have a circuit with a 5 volt power source, a 470 ohm resistor, and an LED. Assume your 5V power supply stops working, but you have a 12V power supply. You want to keep the current at the LED the same. What resistor value would be needed if you changed your power source from 5 volts to 12 volts and, you want to keep the current at the LED the same? Assume that the LED adds no resistance to the current.



Solution ::


$$I_1 = \frac{5}{470} = \frac{1}{94} \approx 0.01064A \quad (1)$$

$$R_1 = \frac{V}{I_1} \quad (2)$$

$$R_1 = \frac{12}{\frac{1}{94}} \quad (3)$$

$$R_1 = 1128 \Omega \quad (4)$$

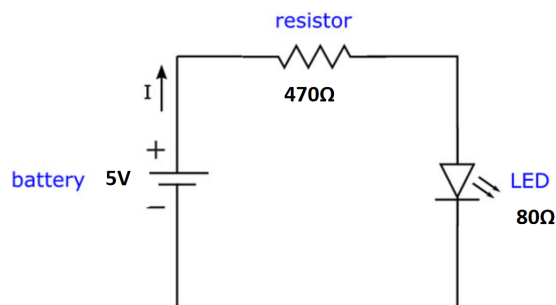Problem 5b. You have a circuit with a 5 volt power source, a 470 ohm resistor, and an LED. However, assume the LED adds a resistance value of 80 ohms to the circuit. As with the previous problem, your 5V power supply stops working, but you have a 12V power supply. You want to keep the current at the LED the same. What resistor value would be needed if you changed your power source from 5 volts to 12 volts and, you want to keep the current at the LED the same?



Solution ::

$$R_T = 470 + 80 = 550 \, \Omega \quad (5)$$

$$I = \frac{V}{R_T} = \frac{5}{550} = 0.009\overline{09}A \quad (6)$$

$$12V \text{ change but same current.} \quad (7)$$

$$R_T = \frac{12}{0.009\overline{09}} = 1320 \, \Omega \quad (8)$$

$$R_1 = R_T - R_{LED} \quad (9)$$

$$R_1 = 1320 - 80 \quad (10)$$

$$R_1 = 1240 \, \Omega \quad (11)$$